



WORLD FIRST !! (maybe)
 Full Wave Rectifier and Full Wave Doubler
 with NO DC CURRENT in the secondary of
 power transformer.
 Many thanks to George Hrischenko VE3DXG
 for the Full Wave Doubler concept.
http://www.kwarc.org/bulletin/99-04/tech_corner.htm
 (c) Giorgio Fontana 2005

use 330uF for 60s rampup,
 good for valves....